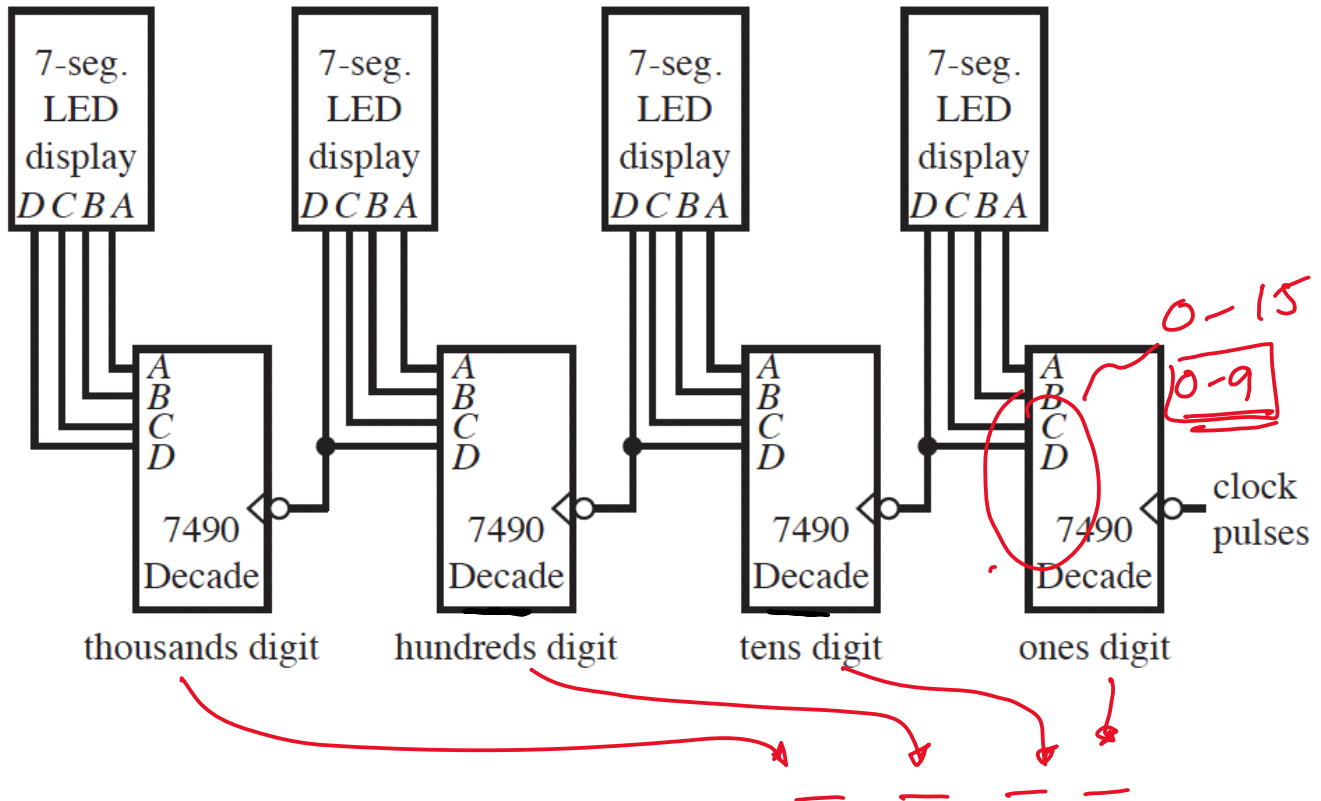


1) Decade Counter




$0-1 - 101P 2^1$
 $0-3 - 201P 2^2$
 $0-7 - 301P 2^3$
 $0-15 - 401P 2^4$

Decade counter (contd)



Table 6.10 7490 decade counter BCD coding

Decimal Count	BCD Output			
	D	C	B	A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
0	0	0	0	0

$2^B + 2^A = 2^1 + 2^0 = 2 + 1 = 3$

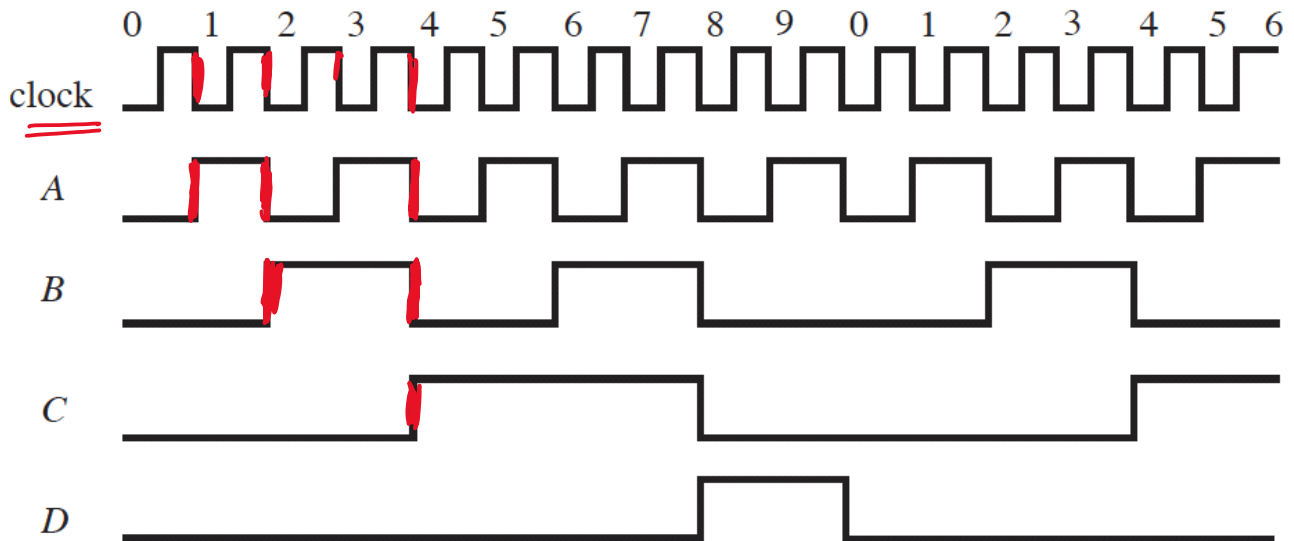

Display

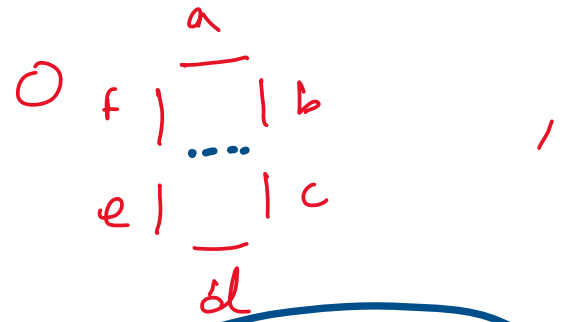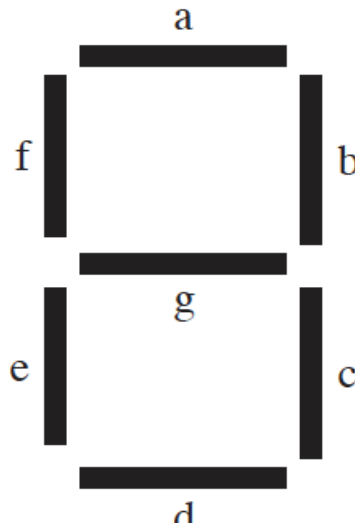

0, 5, 6, 9 = 1
g = 0

0-9
 $\bar{a}, \bar{b}, \bar{c}, \bar{d}, \bar{e}, \bar{f} = 0$
 $\bar{g} = 1$



Table 6.11 7447 BCD to seven-segment decoder

Decimal digit	Input				Output						
	D	C	B	A	\bar{a}	\bar{b}	\bar{c}	\bar{d}	\bar{e}	\bar{f}	\bar{g}
0	0	0	0	0	0	0	0	0	0	0	1
1	0	0	0	1	1	0	0	1	1	1	1
2	0	0	1	0	0	0	1	0	0	1	0
3	0	0	1	1	0	0	0	0	1	1	0
4	0	1	0	0	1	0	0	1	1	0	0
5	0	1	0	1	0	1	0	0	1	0	0
6	0	1	1	0	1	1	0	0	0	0	0
7	0	1	1	1	0	0	0	1	1	1	1
8	1	0	0	0	0	0	0	0	0	0	0
9	1	0	0	1	0	0	0	0	1	0	0


② Schmitt Trigger




Used for switch debouncing

Example

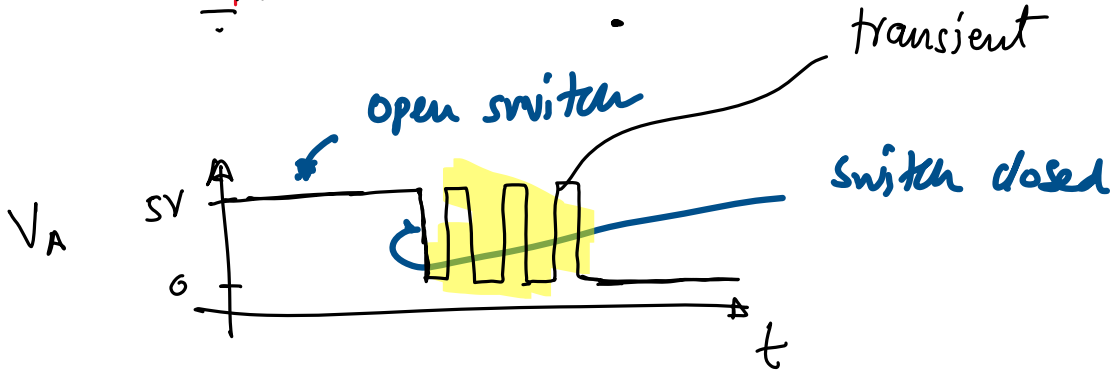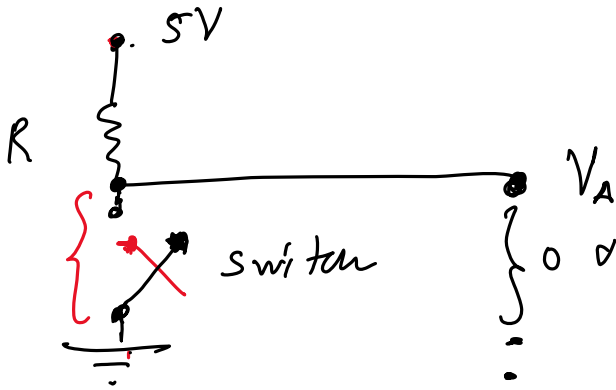

Schmitt trigger prevents this debouncing

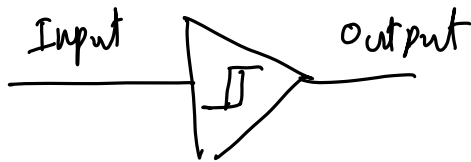


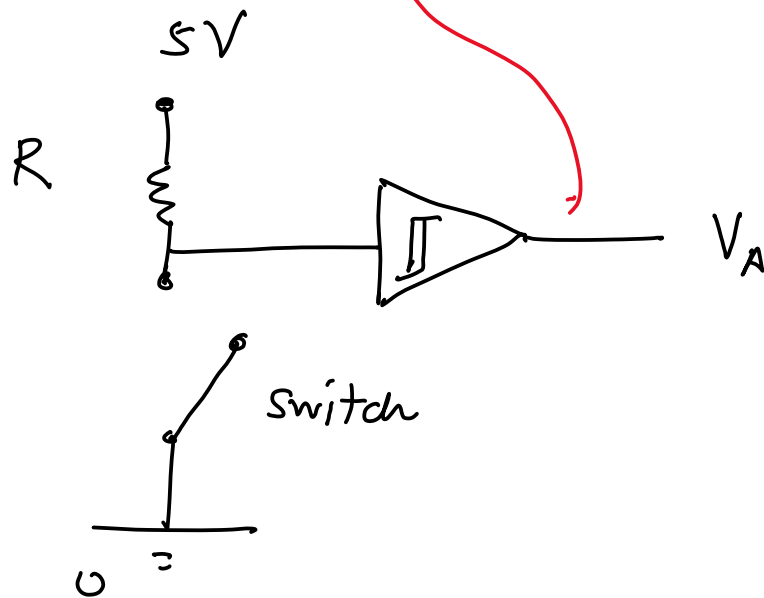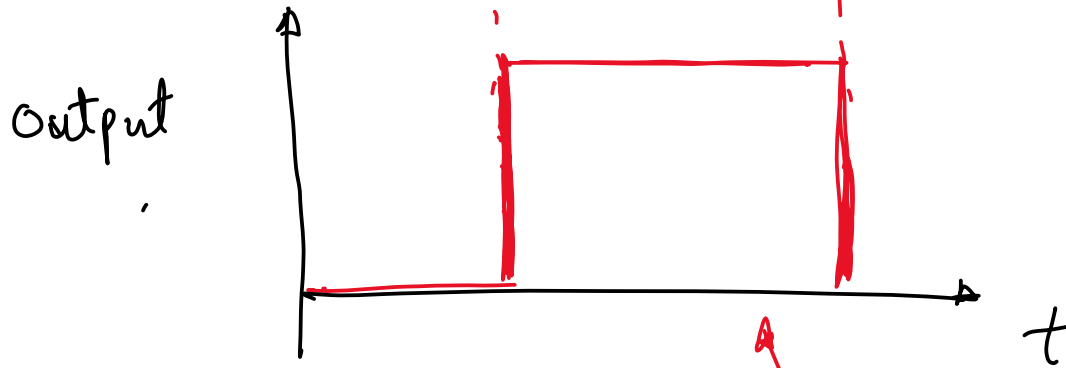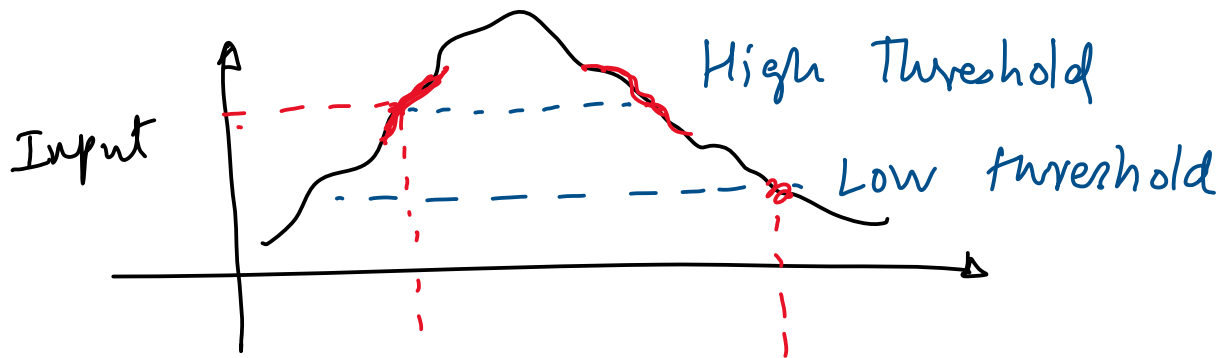


Timer 555

Used for time keeping like a stopwatch.

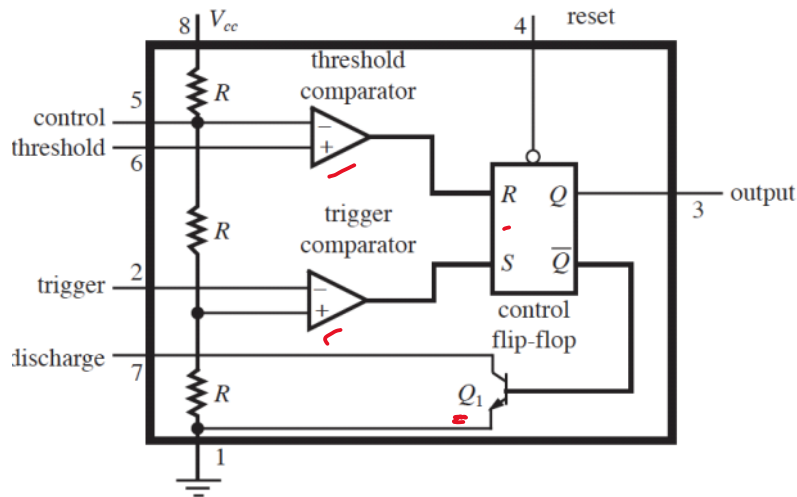Applications: bounce free switches, cascaded timers, frequency dividers, oscillators, LED flashes.



2 op-amps
1 R-S Flip Flop
1 BJT

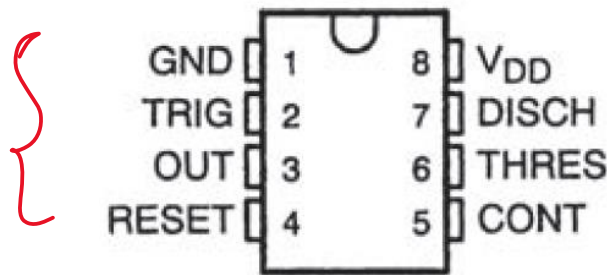

2 modes of operation

- ① Monostable vibrator
- ② Astable vibrator.

Monostable Vibrator (timer)

S	R	Q	\bar{Q}
0	0	Q ₀	\bar{Q}_0
1	0	1	0
0	1	0	1

Working

① Reset is pressed

$R = S = 0$ $Q = 0$; $\bar{Q} = 1$

This turns the BJT ON & drains the capacitor of charge.

② $S = 1$ $R = 0$

$Q = 1$ $\bar{Q} = 0$

→ Thus output = $Q = 1$

③ when $V > \frac{1}{3} V_{cc}$

$S = 0$ $R = 0$

$\bar{Q} = Q_0 = 1$




$Q = \bar{Q}_0 = 0$ } No change in output

④ When capacitor charges to $\frac{2}{3} V_{cc}$,

$R = 1$ $S = 0$

$Q = 0$ $\bar{Q} = 1$

→ output = $Q = 0$

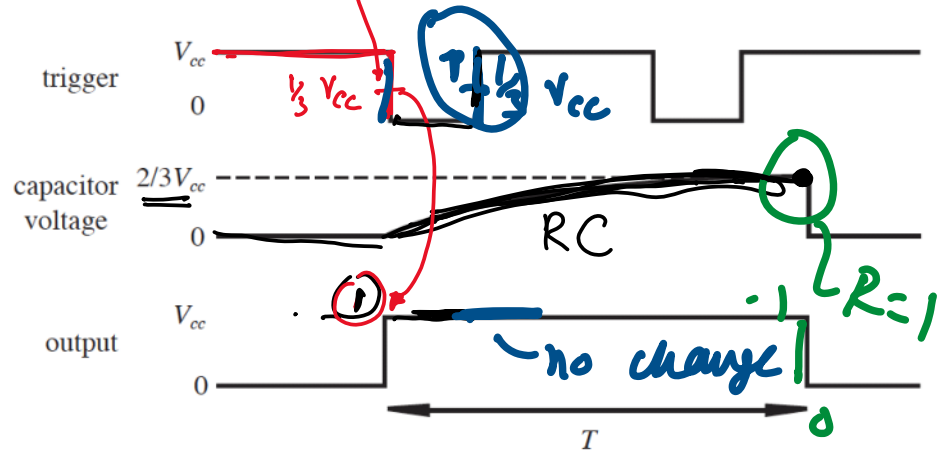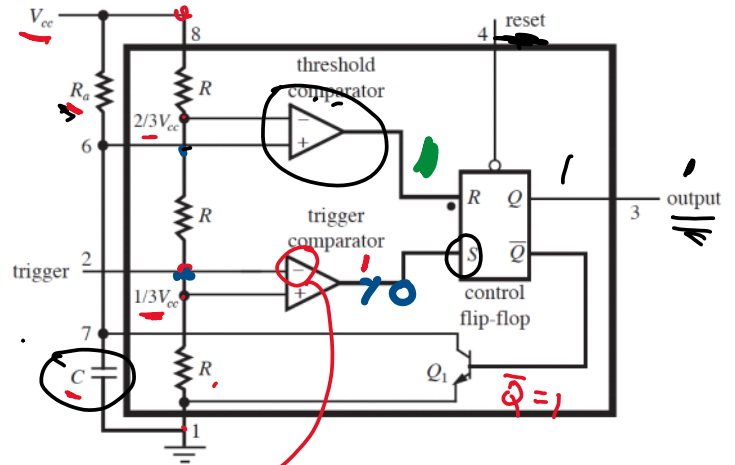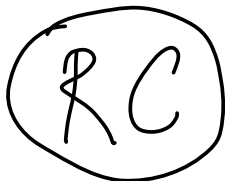

(A) Output is HIGH triggers comparator



(B) Output is LOW

- (i) Capacitor charges
- (ii) Threshold comparator

RC

-
- (i) Capacitors charges
 - (ii) Threshold comparators

Astable multivibrator (timer)

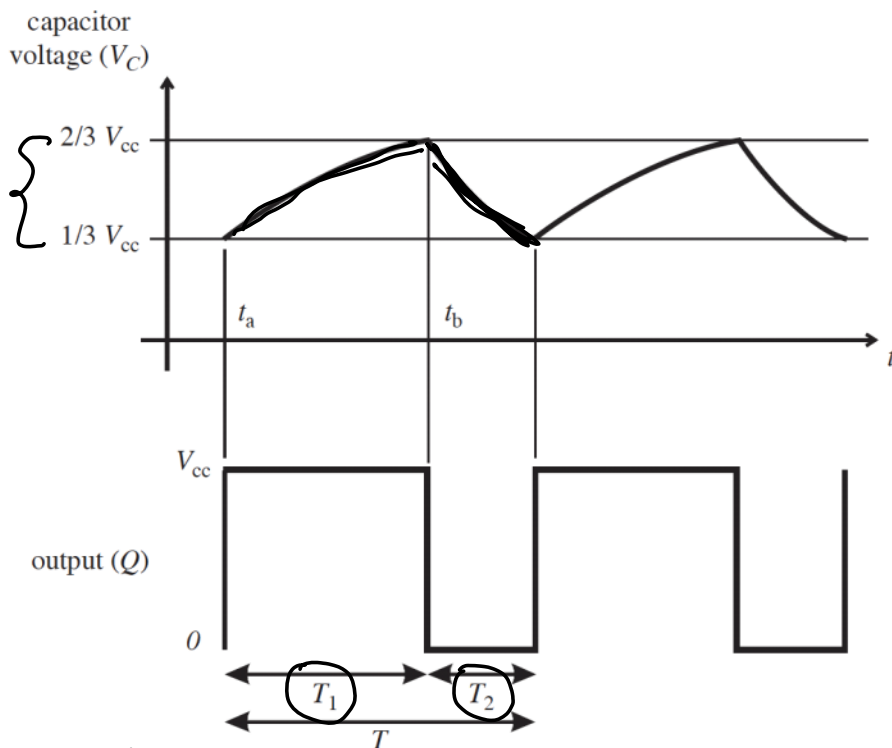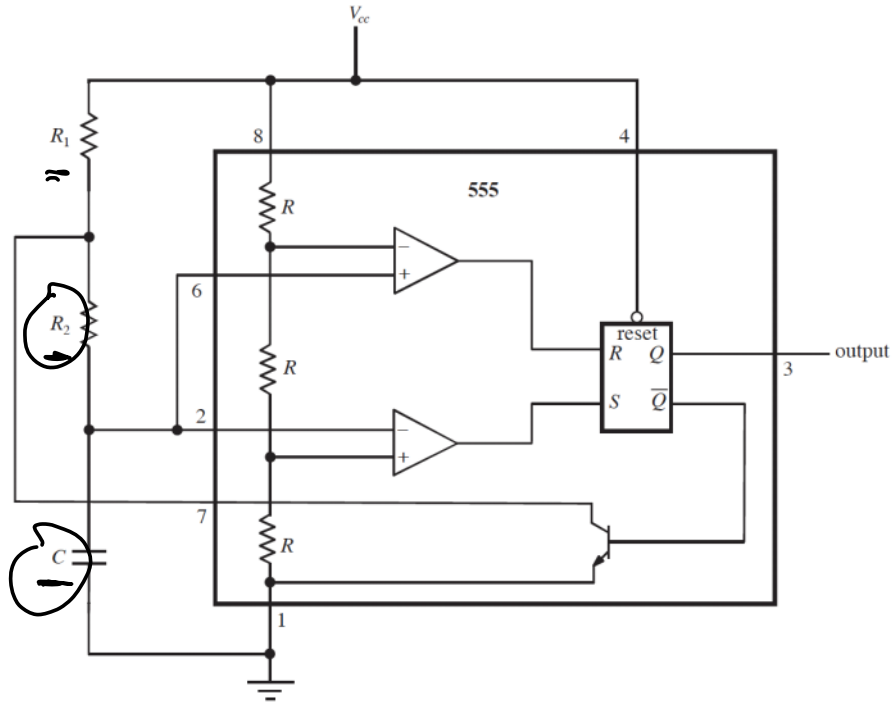

$\rightarrow T_1 = (R_1 + R_2) C$
 $T_2 = R_2 C$